

Problem 4.37

Solution:

Known quantities:

Functions.

Find:

The phasor form.

Analysis:

In phasor form:

a) $V(j\omega) = 155\angle -25^\circ \text{ V}$

b) $V(j\omega) = 5\angle -130^\circ \text{ V}$

c) $I(j\omega) = 10\angle 63^\circ + 15\angle -42^\circ = (4.54 + j8.91) + (11.15 - j10.04) = 15.69 - j1.13 = 15.73\angle -4.12^\circ \text{ A}$

d) $I(j\omega) = 460\angle -25^\circ - 220\angle 75^\circ = (416.90 - j194.40) - (56.94 - j212.50) = 359.96 + j18.10 = 360.4\angle 2.88^\circ \text{ A}$

Problem 4.38

Solution:

Known quantities:

Complex number.

Find:

The polar form.

Analysis:

a) $4 + j4 = 4\sqrt{2}\angle 45^\circ = 5.66\angle 45^\circ$

b) $-3 + j4 = 5\angle 126.9^\circ$

c) $j + 2 - j4 - 3 = -1 - j3 = 3.16\angle -108.4^\circ$

Problem 4.39

Solution:

Known quantities:

Complex number.

Find:

The polar form.

Analysis:

a) $(50 + j10)(4 + j8) = (50.99\angle 11.30^\circ)(8.94\angle 63.43^\circ) = 456.1\angle 74.7^\circ$

$(50 + j10)(4 + j8) = 200 + j400 + j40 + j^2 80 = 120 + j440 = 456.1\angle 74.7^\circ$

b) $(j2 - 2)(4 + j5)(2 + j7) = (2.82\angle 135^\circ)(6.40\angle 51.34^\circ)(7.28\angle 74.05^\circ) = 131.8\angle 260.4^\circ = 131.8\angle -99.6^\circ$

$(j2 - 2)(4 + j5)(2 + j7) = -36 - j126 - j4 - j^2 14 = -22 - j130 = 131.8\angle -99.6^\circ$

Problem 4.40**Solution:****Known quantities:**

Complex number.

Find:

- Complex conjugate
- Polar form, by first multiplying numerator and denominator by the complex conjugate.
- Polar form, by converting into polar coordinates.

Analysis:

$$A = 4 + j4, A^* = 4 - j4$$

$$a) \quad B = 2 - j8, B^* = 2 + j8$$

$$C = -5 + j2, C^* = -5 - j2$$

b)

$$\frac{1+j7}{4+j4} = \frac{(1+j7)(4-j4)}{(4+j4)(4-j4)} = \frac{4-j4+j28-j^2 28}{16+16} = \frac{32+j24}{32} = 1+j0.75 = 1.25\angle 36.87^\circ$$

$$\frac{j4}{2-j8} = \frac{j4(2+j8)}{(2-j8)(2+j8)} = \frac{-32+j8}{4+64} = -\frac{32}{68} + j\frac{8}{68} = 0.485\angle 165.96^\circ$$

$$\frac{1}{-5+j2} = \frac{1(-5-j2)}{(-5+j2)(-5-j2)} = \frac{-5-j2}{25+4} = -\frac{5}{29} - j\frac{2}{29} = 0.1857\angle -158.2^\circ$$

c) Repeat b) converting to polar form first:

$$\frac{1+j7}{4+j4} = \frac{7.071\angle 81.87^\circ}{4\sqrt{2}\angle 45^\circ} = 1.25\angle 36.87^\circ$$

$$\frac{j4}{2-j8} = \frac{4\angle 90^\circ}{8.246\angle 75.96^\circ} = 0.485\angle 165.96^\circ$$

$$\frac{1}{-5+j2} = \frac{1\angle 0^\circ}{5.385\angle 158.2^\circ} = 0.1857\angle -158.2^\circ$$

Problem 4.41**Solution:****Known quantities:**

Complex number.

Find:

Real-imaginary form

Analysis:

$$j^j = e^{-\pi/2} = 0.2079$$

$$e^{j\pi} = \cos(\pi) + j\sin(\pi) = -1 + j0 = -1$$

Section 4.4: Phasor Solution of Circuits with Sinusoidal Excitation

Focus on Methodology: Phasors

- Any sinusoidal signal may be mathematically represented in one of two ways: a **time domain form**: $v(t) = A \cos(\omega t + \theta)$, and a **frequency domain form**: $V(j\omega) = Ae^{j\theta} = A\angle\theta$. Note the $j\omega$ in the notation $V(j\omega)$, indicating the $e^{j\omega t}$ dependence of the phasor. In the remainder of this chapter, bold uppercase quantities indicate phasor voltages and currents.
- A phasor is a complex number, expressed in polar form, consisting of a **magnitude** equal to the peak amplitude of the sinusoidal signal and a **phase angle** equal to the phase shift of the sinusoidal signal *referenced to a cosine signal*.
- When using phasor notation, it is important to note the specific frequency ω of the sinusoidal input.

Problem 4.43

Solution:

Known quantities:

The current through and the voltage across a component.

Find:

- Whether the component is a resistor, capacitor, inductor
- The value of the component in ohms, farads, or henrys.

Analysis:

- The current and the voltage can be expressed in phasor form:

$$\mathbf{I} = 17\angle -15^\circ \text{ mA}, \quad \mathbf{V} = 3.5\angle 75^\circ \text{ V}$$

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{3.5\angle 75^\circ \text{ V}}{17\angle -15^\circ \text{ mA}} = 205.9\angle 90^\circ \Omega = 0 + j \cdot 205.9 \Omega$$


The impedance has a positive imaginary or reactive component and a positive angle of 90 degree indicating that this is an inductor (see Fig. 4.39).

$$\text{b) } \mathbf{Z}_L = j \cdot X_L = j \cdot \omega L = j \cdot 205.9 \Omega \Rightarrow L = \frac{205.9 \Omega}{628.3 \frac{\text{rad}}{\text{s}}} = 327.7 \text{ m} \frac{\text{Vs}}{\text{A}} = 327.7 \text{ mH}$$

Problem 4.47**Solution:****Known quantities:**

The values of the impedance, $R_1 = 2.3 \text{ k}\Omega$, $R_2 = 1.1 \text{ k}\Omega$, $L = 190 \text{ mH}$, $C = 55 \text{ nF}$ and the voltage applied to the circuit shown in Figure P4.47, $v_s(t) = 7 \cos(3000t + 30^\circ) \text{ V}$.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

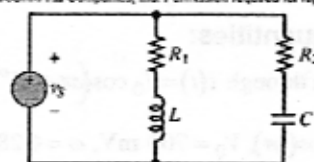**Find:**

The equivalent impedance of the circuit.

Analysis:

$$X_L = \omega L = \left(3 \text{ k} \frac{\text{rad}}{\text{s}}\right)(190 \text{ mH}) = 0.57 \text{ k}\Omega \Rightarrow Z_L = +j \cdot X_L = +j \cdot 0.57 \text{ k}\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{\left(3 \text{ k} \frac{\text{rad}}{\text{s}}\right)(55 \text{ nF})} = 6.061 \text{ k}\Omega \Rightarrow Z_C = -j \cdot X_C = -j \cdot 6.061 \text{ k}\Omega$$

$$Z_{eq1} = Z_{R1} + Z_L = R_1 + jX_L = 2.3 + j \cdot 0.57 \text{ k}\Omega = 2.37 \angle 13.92^\circ \text{ k}\Omega$$

$$Z_{eq2} = Z_{R2} + Z_C = R_2 - jX_C = 1.1 - j \cdot 6.061 \text{ k}\Omega = 6.16 \angle -79.71^\circ \text{ k}\Omega$$

$$Z_{eq} = \frac{Z_{eq1} \cdot Z_{eq2}}{Z_{eq1} + Z_{eq2}} = \frac{(2.37 \angle 13.92^\circ \text{ k}\Omega)(6.16 \angle -79.71^\circ \text{ k}\Omega)}{(2.3 + j \cdot 0.57 \text{ k}\Omega) + (1.1 - j \cdot 6.061 \text{ k}\Omega)} = \frac{14.60 \angle -65.79^\circ \text{ k}\Omega^2}{3.4 - j \cdot 5.491 \text{ k}\Omega} = \frac{14.60 \angle -65.79^\circ \text{ k}\Omega^2}{6.458 \angle -58.23^\circ \text{ k}\Omega} = 2.261 \angle -7.56^\circ \text{ k}\Omega$$

Problem 4.48**Solution:****Known quantities:**

The values of the impedance, $R_1 = 3.3 \text{ k}\Omega$, $R_2 = 22 \text{ k}\Omega$, $L = 1.90 \text{ H}$, $C = 6.8 \text{ nF}$ and the voltage applied to the circuit shown in Figure P4.47, $v_s(t) = 636 \cos(3000t + 15^\circ) \text{ V}$.

Find:

The equivalent impedance of the circuit.

Analysis:

$$X_L = \omega L = \left(3 \text{ k} \frac{\text{rad}}{\text{s}}\right)(1.90 \text{ H}) = 5.7 \text{ k}\Omega \Rightarrow Z_L = +j \cdot X_L = +j \cdot 5.7 \text{ k}\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{\left(3 \text{ k} \frac{\text{rad}}{\text{s}}\right)(6.8 \text{ nF})} = 49.02 \text{ k}\Omega \Rightarrow Z_C = -j \cdot X_C = -j \cdot 49.02 \text{ k}\Omega$$

$$Z_{eq1} = Z_{R1} + Z_L = R_1 + jX_L = 3.3 + j \cdot 5.7 \text{ k}\Omega = 6.59 \angle 59.93^\circ \text{ k}\Omega$$

$$Z_{eq2} = Z_{R2} + Z_C = R_2 - jX_C = 22 - j \cdot 49.02 \text{ k}\Omega = 53.73 \angle -65.83^\circ \text{ k}\Omega$$

Problem 4.53**Solution:****Known quantities:**

The values of the impedance, $R_s = 50\ \Omega$, $R_c = 40\ \Omega$, $L = 20\ \mu\text{H}$, $C = 1.25\ \text{nF}$, and the voltage applied to the circuit shown in Figure P4.53,

$$v_s(t) = V_0 \cos(\omega t + 0^\circ) \quad V_0 = 10\ \text{V}, \quad \omega = 6\ \text{M} \frac{\text{rad}}{\text{s}}.$$

Find:

The current supplied by the source.

Analysis:

Assume clockwise currents:

$$X_L = \omega L = \left(6\ \text{M} \frac{\text{rad}}{\text{s}}\right)(20\ \mu\text{H}) = 1203\ \Omega \Rightarrow Z_L = 0 + j120\ \Omega = 120\angle 90^\circ\ \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{\left(6\ \text{M} \frac{\text{rad}}{\text{s}}\right)(1.25\ \text{nF})} = 133.3\ \Omega \Rightarrow Z_C = 0 - j133.3\ \Omega = 133.3\angle -90^\circ\ \Omega$$

$$Z_{R_c} = 40 - j\ \Omega = 40\angle 0^\circ\ \Omega, \quad Z_{R_s} = 50 - j\ \Omega = 50\angle 0^\circ\ \Omega$$

Equivalent impedances:

$$Z_{eq1} = Z_{R_c} + Z_L = 40 + j120\ \Omega = 126.5\angle 71.56^\circ\ \Omega$$


$$\begin{aligned} Z_{eq} &= Z_{R_s} + \frac{Z_C \cdot Z_{eq1}}{Z_C + Z_{eq1}} = 50 + j0\ \Omega + \frac{(133.3\angle -90^\circ\ \Omega)(126.5\angle 71.56^\circ\ \Omega)}{133.3\angle -90^\circ\ \Omega + 126.5\angle 71.56^\circ\ \Omega} \\ &= 50 + j0\ \Omega + \frac{16.87\angle -18.44^\circ\ \text{k}\Omega^2}{42.161\angle -18.44^\circ\ \Omega} = 50\angle 0^\circ\ \Omega + 400\angle 0^\circ\ \Omega = 450\angle 0^\circ\ \Omega \end{aligned}$$

$$\text{OL:} \quad I_s = \frac{V_s}{Z_{eq}} = \frac{10\angle 0^\circ\ \text{V}}{450\angle 0^\circ\ \Omega} = 22.22\angle 0^\circ\ \text{mA} \Rightarrow i_s(t) = 22.22 \cos(\omega t + 0^\circ)\ \text{mA}$$

Note:

The equivalent impedance of the parallel combination is purely resistive; therefore, the frequency given is the resonant frequency of this network.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

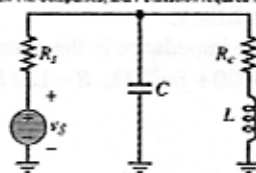

Problem 4.71**Solution:****Known quantities:**

Circuit shown in Figure P4.71 the values of the impedance, $L = 0.1$ H, capacitance, $C = 100$ μ F, and the voltage source $v_{in}(t) = 12 \cos(10t)$ V.

Find:

The Thévenin equivalent of the circuit as seen by the load resistor R_L .

Analysis:

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j10 \frac{\text{rad}}{\text{s}} \cdot 100 \mu\text{F}} = -j1000 \Omega$$

$$Z_L = j\omega L = j10 \frac{\text{rad}}{\text{s}} \cdot 0.1 \text{ H} = j1 \Omega$$


The equivalent impedance is:

$$Z_T = Z_L \parallel Z_C = \frac{Z_L \cdot Z_C}{Z_L + Z_C} = \frac{j(-j1000)}{j - j1000} = \frac{1000}{-j999} = 1.001 \angle 90^\circ \Omega = j1.001 \Omega$$

The Thévenin voltage is:

$$V_T = \frac{Z_C}{Z_L + Z_C} V_{in} = \frac{-j1000}{j - j1000} \cdot 12 \angle 0^\circ = \frac{1000}{999} \cdot 12 \angle 0^\circ = 12.012 \angle 0^\circ \text{ V}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

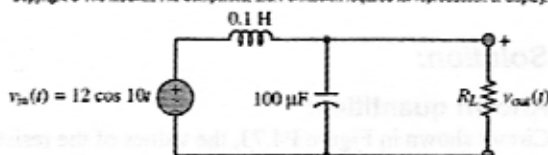**Problem 4.72****Solution:****Known quantities:**

Circuit shown in Figure P4.72 the values of the resistance, $R_1 = 4 \Omega$, $R_2 = 4 \Omega$, capacitance, $C = 1/4$ F, inductance, $L = 2$ H, and the voltage source $v_s(t) = 2 \cos(2t)$ V.

Find:

The current in the circuit $i_L(t)$ using phasor techniques.

Analysis:

$$V_S(t) = 2 \angle 0^\circ \text{ V}$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j2 \frac{1}{4}} = -j2 \Omega$$

$$Z_L = j\omega L = j2 \cdot 2 = j4 \Omega$$

Applying the voltage divider rule:


$$V_L = \frac{(Z_L \parallel (Z_C + Z_2))}{Z_1 + (Z_L \parallel (Z_C + Z_2))} V_S = \frac{4 \angle 36.8^\circ}{4 \angle 0^\circ + 4 \angle 36.8^\circ} 2 \angle 0^\circ = 1.05 \angle 18.4^\circ \text{ V}$$

Therefore, the current is:

$$I_L = \frac{V_L}{Z_L} = \frac{1.05 \angle 18.4^\circ}{4 \angle 90^\circ} = 0.2635 \angle -71.6^\circ \text{ A}$$

$$i_L(t) = 0.2635 \cos(2t - 71.6^\circ) \text{ A}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

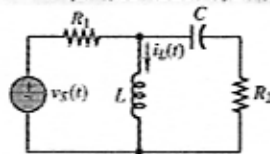

Problem 4.74**Solution:****Known quantities:**

Circuit shown in Figure P4.74, the values of the resistance, $R_1 = 40 \, \Omega$, $R_2 = 10 \, \Omega$, capacitance, $C = 500 \, \mu\text{F}$, inductance, $L = 0.2 \, \text{H}$, and the current source

$$i_s(t) = 40 \cos(100t) \, \text{A}.$$

Find:

The voltages in the circuit $v_1(t)$ and $v_2(t)$.

Analysis:

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{100 \cdot 500 \cdot 10^{-6}} = -j20 \, \Omega,$$

$$Z_L = j\omega L = j100 \cdot 0.2 = j20 \, \Omega$$

Applying KCL at node 1, we have:

$$I_s = \frac{V_1}{R_1} + \frac{V_1 - V_2}{Z_C} \Rightarrow I_s = \left(\frac{1}{R_1} + \frac{1}{Z_C} \right) V_1 - \frac{1}{Z_C} V_2 \Rightarrow 40 \angle 0^\circ = \left(\frac{1}{40} + \frac{j}{20} \right) V_1 - \frac{j}{20} V_2$$

Applying KCL at node 2, we have

$$\frac{V_1 - V_2}{Z_C} = \frac{V_2}{R_2} + \frac{V_2}{Z_L} \Rightarrow \frac{V_1}{Z_C} = \left(\frac{1}{R_2} + \frac{1}{Z_L} + \frac{1}{Z_C} \right) V_2 \Rightarrow j \frac{V_1}{20} = \left(\frac{1}{10} - j \frac{1}{20} + j \frac{1}{20} \right) V_2$$

Therefore:


$$\begin{cases} 40 \angle 0^\circ = \left(\frac{1}{40} + \frac{j}{20} \right) V_1 - \frac{j}{20} V_2 \\ j \frac{V_1}{20} = \left(\frac{1}{10} \right) V_2 \end{cases} \Rightarrow \begin{cases} 40 \angle 0^\circ = \left(\frac{1}{40} + \frac{j}{20} \right) (-j2V_2) - \frac{j}{20} V_2 \\ V_1 = -j2V_2 \end{cases}$$

$$\begin{cases} 40 \angle 0^\circ = -\frac{j}{20} V_2 + \frac{1}{10} V_2 - \frac{j}{20} V_2 = \left(\frac{1}{10} - \frac{j}{10} \right) V_2 \\ V_1 = -j2V_2 \end{cases}$$

$$V_2 = \frac{40 \angle 0^\circ}{\left(\frac{1}{10} - \frac{j}{10} \right)} = 282.84 \angle 45^\circ \, \text{V}, \quad V_1 = -j2V_2 = 565.68 \angle -45^\circ \, \text{V}$$

$$v_2(t) = 282.84 \cos(100t + 45^\circ) \, \text{V}, \quad v_1(t) = 565.68 \cos(100t - 45^\circ) \, \text{V}$$

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

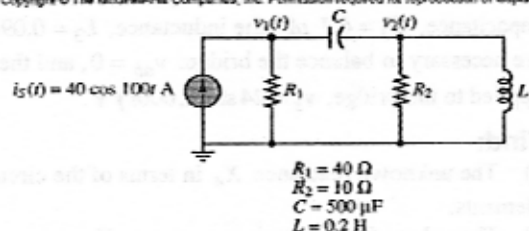

Problem 4.76**Solution:****Known quantities:**

Circuit shown in Figure P4.72, the values of the resistance, $R_1 = 4 \Omega$, $R_2 = 4 \Omega$, capacitance, $C = 1/4 \text{ F}$, inductance, $L = 2 \text{ H}$, and the voltage source $v_s(t) = 2 \cos(2t) \text{ V}$.

Find:

The Thévenin impedance seen by resistor R_2 .

Analysis:

$$Z_T = (R_1 \parallel Z_L) + (Z_C) = (4 \parallel j2) + (-j2) = j2(1-j) - j2 = 2 + j2 + (-j2) = 2 \Omega$$

Problem 4.77**Solution:****Known quantities:**

Circuit shown in Figure P4.74, the values of the resistance, $R_1 = 10 \Omega$, $R_2 = 40 \Omega$, capacitance, $C = 500 \mu\text{F}$, inductance, $L = 0.2 \text{ H}$, and the current source $i_s(t) = 40 \cos(100t) \text{ A}$.

Find:

The Thévenin voltage seen by inductance L .

Analysis:

The Thévenin equivalent voltage source is the open-circuit voltage at the load terminals:

$$V_T = R_2 I_2 = 40 I_2$$

From the current division, we have

$$I_2 = \frac{R_1}{(R_2 + Z_C) + R_1} I_S = \frac{10}{(40 - j20) + 10} 40 \angle 0^\circ = 7.43 \angle 21.8^\circ \text{ A}$$

$$V_T = R_2 I_2 = 40 \cdot 7.43 \angle 21.8^\circ = 297 \angle 21.8^\circ \text{ V}$$

$$v_T(t) = 297 \cos(100t + 21.8^\circ) \text{ V}$$

Problem 4.78

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Solution:**Known quantities:**

Circuit shown in Figure P4.78, the values of the impedance, $R = 8 \Omega$, $Z_C = -j8 \Omega$, $Z_L = j8 \Omega$, and the voltage source $V_s = 5 \angle -30^\circ \text{ V}$.

Find:


The Thévenin equivalent circuit seen from the terminals a-b.

Analysis:

The Thévenin equivalent circuit is given by:

$$V_{TH} = \left(\frac{8 + j8}{8 + j8 - j8} \right) 5 \angle -30^\circ = (1 + j) 5 \angle -30^\circ = 7.07 \angle 15^\circ \text{ V}$$
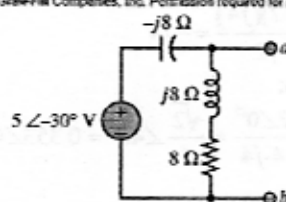
$$Z_{TH} = \frac{(8 + j8)(-j8)}{8 + j8 - j8} = (8 - j8) = 8\sqrt{2} \angle -45^\circ \Omega$$



Handwritten notes: $V_{ad} = 7.85$, $8\sqrt{2} = 11.3$